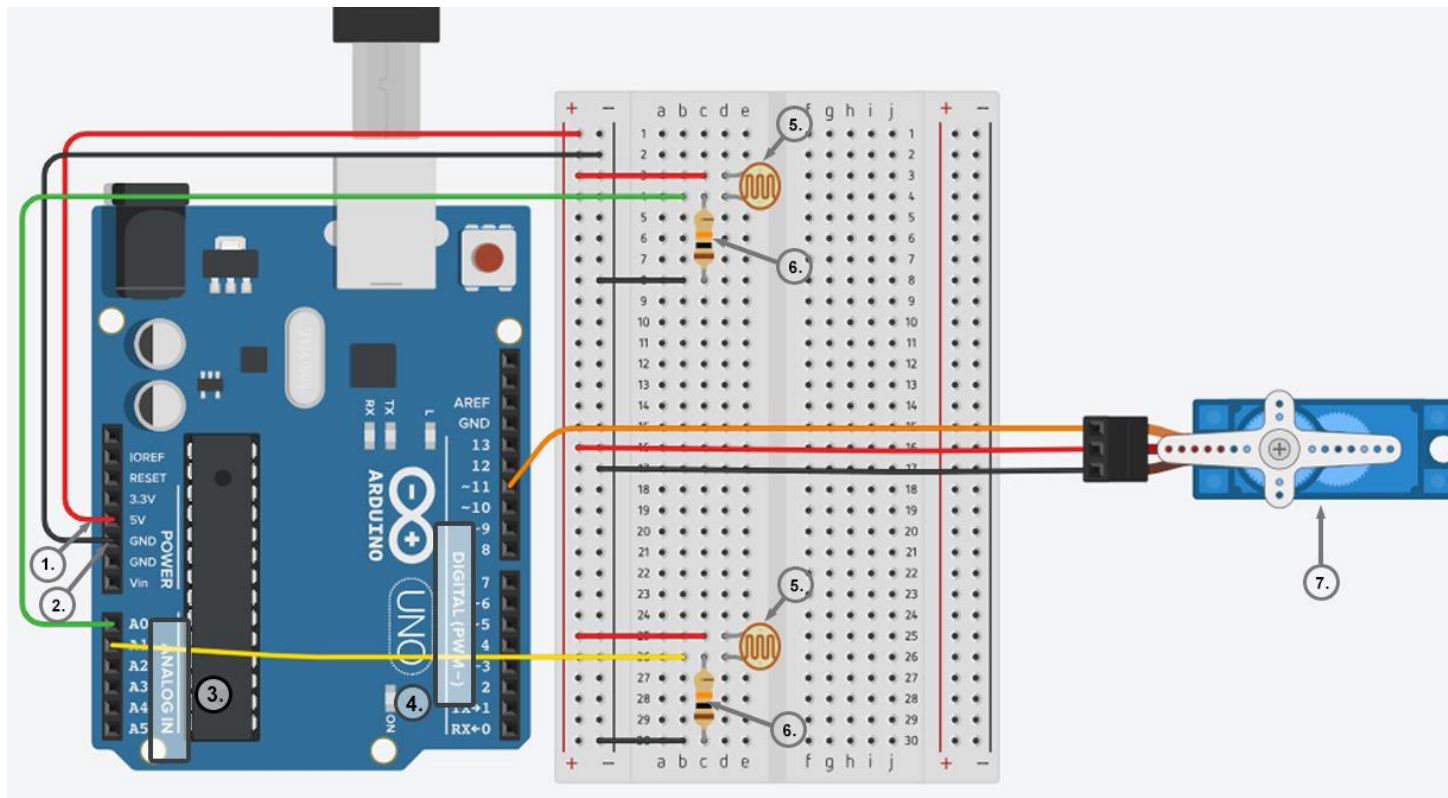


The sunflower moves towards the direction of light



- Use 5V (1) and Ground/ GND (2) pins to respectively provide 5V power and ground to your breadboard
- Connect one of photoresistor's (5) legs to power (5V), and the other to one of the analog pins (3) (pin A0 in the example), as well as to ground through the 10KΩ resistor (6). Repeat the same procedure for the second photoresistor.
- Connect the orange colored pin of the servo motor (7) to one of the digital pins (4) (digital pin 11 in the example), the red one to power (5V) and the brown one to ground.

Notes: