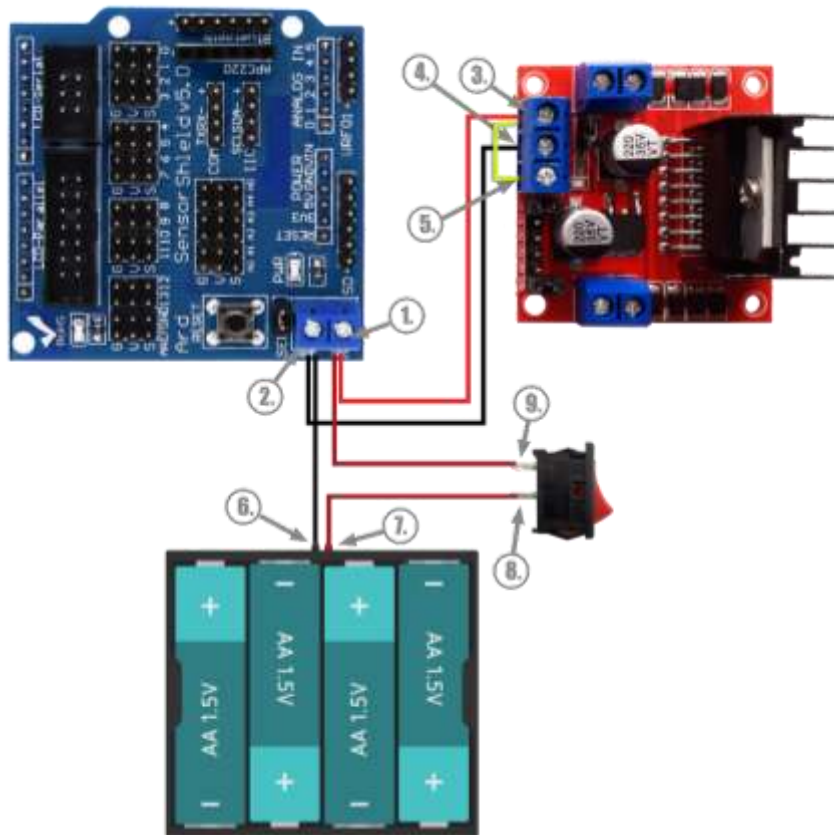


## Connecting the battery holder and the switch to supply power



This diagram presents how to provide the circuit with an extra source of power, by using a 4-AA battery holder with free wires and an on-off switch.

- Connect the ground of the battery holder (6.) to Shield's ground (2.).
- Connect the 5V (7.) of the battery holder to Shield's 5V (1.) through the two pins (8., 9.) of the switch.

Notes:

*You will probably need a wire stripper or a cutter and a soldering iron or a hot glue gun for connecting the switch to the circuit.*

*A small screwdriver might also be useful for connecting the wires of battery holder to Arduino Sensor Shield.*

Notes: