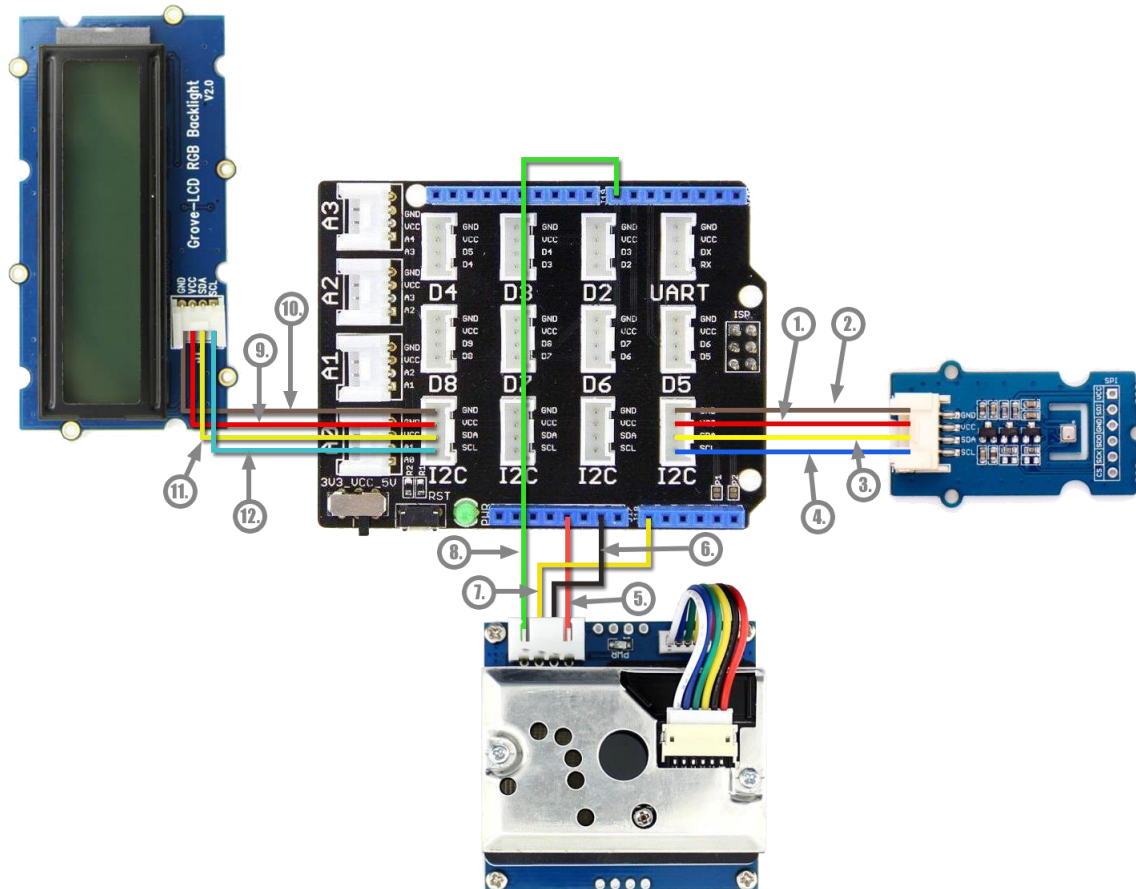


Connecting the Grove LCD RGB display



This diagram presents how the Grove LCD RGB display is connected to Grove Base Shield. For your convenience you are advised to use a 4-pin F-F Grove wire, and make sure that:

- The VCC pin (9.) is connected to the Vcc pin of I2C port.
- The GND pin (10.) is connected to the GND pin of I2C port.
- The SDA pin (11.) is connected to the SDA pin of I2C port.
- The SCL pin (12.) is connected to the SCL pin of I2C port.

Notes:

*The colors of the wires in the diagram are indicative. The Grove wires might come in different colors.*

Notes: